

NAME - ATHARVA BHATT

ROLL NO - 20095019

BRANCH - ELECTRONICS ENGINEERING

E0203 - MID TERM EXAM

Q.1.

$$(a) \quad F(A, B, C, D) = \sum m(0, 1, 5, 6, 8, 10, 12, 15)$$

$$\begin{aligned} \therefore F = & \underbrace{\bar{A}\bar{B}\bar{C}\bar{D}}_0 + \underbrace{\bar{A}\bar{B}\bar{C}D}_1 + \underbrace{\bar{A}B\bar{C}D}_5 \\ & + \underbrace{\bar{A}BC\bar{D}}_6 + \underbrace{A\bar{B}\bar{C}\bar{D}}_8 + \underbrace{A\bar{B}C\bar{D}}_{10} \\ & + \underbrace{AB\bar{C}\bar{D}}_{12} + \underbrace{ABC\bar{D}}_{15} \end{aligned}$$


$$\begin{aligned} F = & \bar{A} [\bar{B}\bar{C}\bar{D} + \bar{B}\bar{C}D + B\bar{C}D + BC\bar{D}] \\ & + A [\bar{B}\bar{C}\bar{D} + \bar{B}CD + B\bar{C}\bar{D} + BCD] \end{aligned}$$

$$\text{Now, } A + \bar{A} = 1 \quad \{ \text{Complement Law} \}$$

$$\begin{aligned} \therefore F = & (1) \underbrace{\bar{B}\bar{C}\bar{D}}_0 + \bar{A} [\underbrace{\bar{B}\bar{C}D}_1 + \underbrace{B\bar{C}D}_5 + \underbrace{BC\bar{D}}_6] \\ & + A [\underbrace{\bar{B}CD}_2 + \underbrace{B\bar{C}\bar{D}}_4 + \underbrace{B\bar{C}D}_7] \end{aligned}$$

- Therefore, the selection lines will be B (MSB), C and D and the input lines will be, $I_0 = 1$ (V_{cc}), $I_1 = \bar{A}$, $I_2 = A$, $I_3 = 0$ (ground), $I_4 = A$, $I_5 = \bar{A}$, $I_6 = \bar{A}$, $I_7 = A$. for the $8:1$ MUX.

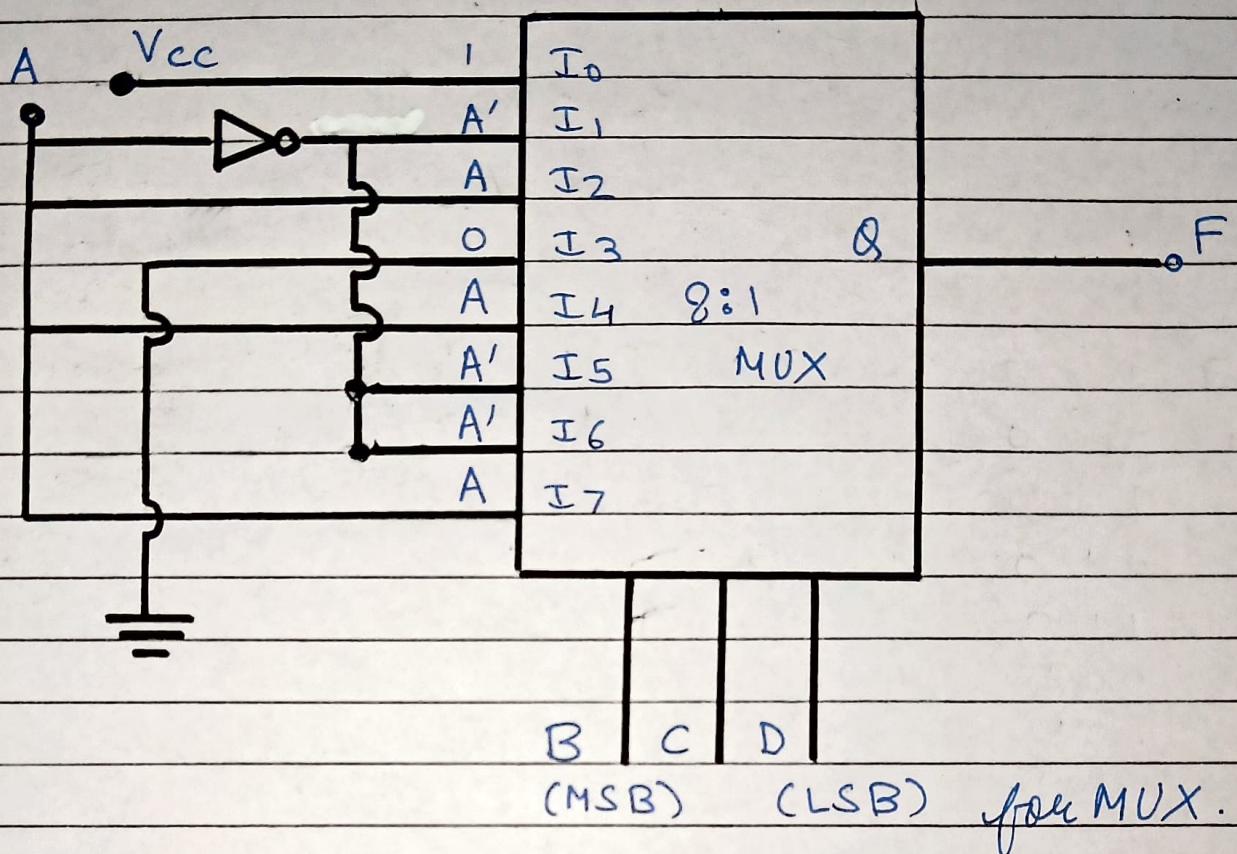\Rightarrow Thus, the implementation using 8:1 MUX is,



(b) The 2's complement representation for decimal number (-28) is 2's complement of decimal number (28).

Now, 16-bit binary representation of decimal number (28) is

0000 0000 0001 1100

\therefore 1's complement : 1111 1111 1110 0011

$$\begin{aligned} \therefore 2's \text{ complement} &: 1111 1111 1110 0011 + 1 \\ &= \underline{\underline{1111 1111 1110 0100}} \quad (-28) \end{aligned}$$

\Rightarrow The 16-bit 2's complement representation for decimal number (-28) is,

$\underline{\underline{1111 1111 1110 0100}}$.

3

(c) To convert Binary to Gray Code:

- In the Gray code, the MSB will be the same as the MSB of the given binary number.
 - Now, to get the 2nd bit of the Gray code, we perform exclusive-or (XOR) of the 1st and 2nd bit of the binary number.
 - Similarly, the n^{th} bit of Gray code ($n \geq 1$) is the XOR of $(n-1)^{\text{th}}$ and n^{th} bit of the binary number.

Now, the given binary number is 1011,

∴ MSB of Gray Code = 1,

$$\therefore \text{2}^{\text{nd}} \text{ bit of Gray Code} = 1 \oplus 0 = 1$$

1st \oplus 2nd bit (binary)

$$\therefore \text{3rd bit of Gray Code} = 0 \oplus 1 = 1$$

2nd \oplus 3rd bit (binary)

$$\therefore 4^{\text{th}} \text{ bit of Gray Code} = \begin{matrix} 1 \\ 3^{\text{rd}} \end{matrix} \oplus \begin{matrix} 1 \\ 4^{\text{th}} \end{matrix} = 0$$


bit (binary)

∴ Gray Code form is 1110.

\Rightarrow The binary number 1011 in the form of Gray code is:

1110 ..

Q.2.

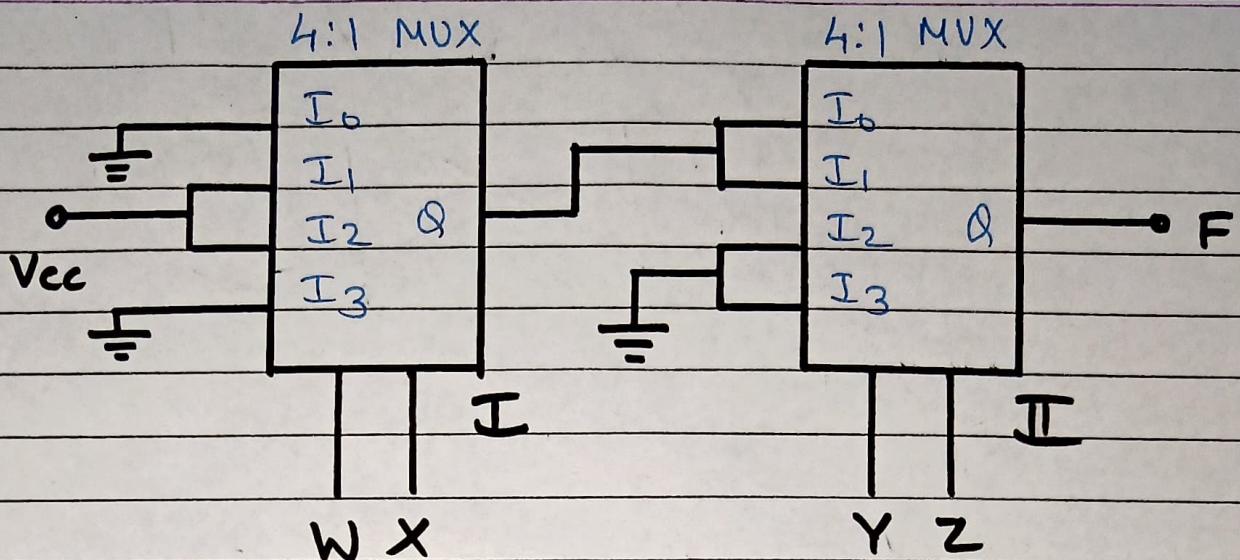

Function Table.

W	X	Q _I	Y	Z	Q _{II}
0	0	I ₀ (I)	0	0	I ₀ (II)
0	1	I ₁ (I)	0	1	I ₁ (II)
1	0	I ₂ (I)	1	0	I ₂ (II)
1	1	I ₃ (I)	1	1	I ₃ (II)

∴ The boolean expression for Q_I is :

$$Q_I = \bar{W}\bar{X}(I_0(I)) + \bar{W}X(I_1(I)) \\ + W\bar{X}(I_2(I)) + WX(I_3(I))$$

$$\left. \begin{array}{l} I_0 = GND \equiv 0, I_1 = V_{cc} \equiv 1, I_2 = V_{cc} \equiv 1, \\ I_3 = GND \equiv 0 \end{array} \right\}$$

$$\therefore Q_I = \bar{W}X + W\bar{X} = W \oplus X \quad \text{--- (1)}$$

Now, the boolean expression for Q_{II} is :

$$Q_{II} = \bar{Y}\bar{Z}(I_0(II)) + \bar{Y}Z(I_1(II)) \\ + Y\bar{Z}(I_2(II)) + YZ(I_3(II))$$

$$\{ I_0 = I_1 = Q_I, I_2 = I_3 = GND \equiv 0 \}$$

$$\therefore Q_{II} = \bar{Y}\bar{Z}Q_I + \bar{Y}ZQ_I, \text{ from (1),}$$

$$\therefore Q_{II} = \bar{Y}\bar{Z}(\bar{W}x + W\bar{x}) + \bar{Y}Z(\bar{W}x + W\bar{x})$$

$$\therefore Q_{II} = \bar{W}x\bar{Y}\bar{Z} + W\bar{x}\bar{Y}\bar{Z} + \bar{W}x\bar{Y}Z + W\bar{x}\bar{Y}Z.$$

$$\therefore Q_{II} = \underline{\leq m(4, 5, 8, 9)} = F$$

(W, X, Y, Z)

YZ

WX	00	01	11	10
00	0 ₀	0 ₁	0 ₃	0 ₂
01	1 ₄	1 ₅	0 ₇	0 ₆
11	0 ₁₂	0 ₁₃	0 ₁₅	0 ₁₄
10	1 ₈	1 ₉	0 ₁₁	0 ₁₀

K-Map.

$$\therefore F = \underline{\bar{W}\bar{x}\bar{Y}} + \underline{\bar{W}x\bar{Y}}$$


\Rightarrow The minimized Boolean expression corresponding to output F is,

$$F = \bar{W}\bar{x}\bar{Y} + \bar{W}x\bar{Y} = (\bar{W} \oplus x)\bar{Y}$$

$$\Rightarrow F = (\bar{W} \oplus x)\bar{Y}$$

$$\left\{ \begin{array}{l} \bar{W}\bar{x} + \bar{W}x \\ = \bar{W} \oplus x \end{array} \right\}$$

Q.3.

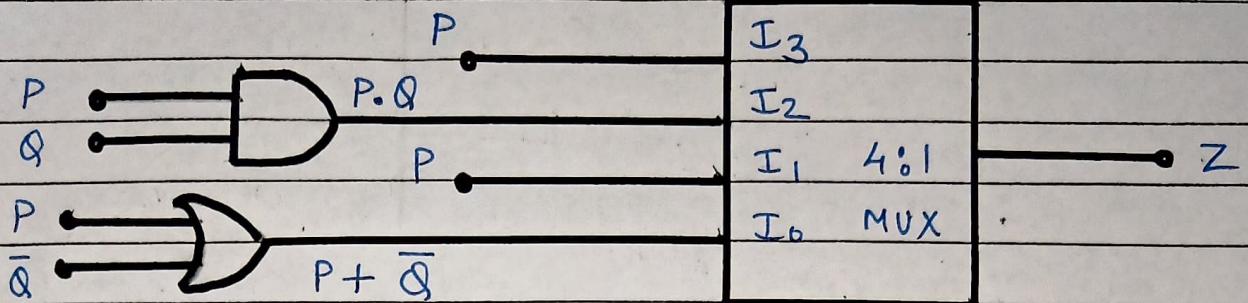

R	S	Z
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

Function Table

∴ the Boolean expression is given by :

$$Z = \bar{R}\bar{S}(I_0) + \bar{R}S(I_1) + R\bar{S}(I_2) + RS(I_3)$$

$$\therefore Z = RS(P) + R\bar{S}(P.Q) + \bar{R}S(P) + \bar{R}\bar{S}(P+\bar{Q})$$

$$= PRS + P\bar{Q}R\bar{S} + P\bar{R}S + P\bar{R}\bar{S} + \bar{Q}\bar{R}\bar{S}$$

$$= PRS(Q+\bar{Q}) + P\bar{Q}R\bar{S} + P\bar{R}S(Q+\bar{Q})$$

$$+ P\bar{R}\bar{S}(Q+\bar{Q}) + \bar{Q}\bar{R}\bar{S}(P+\bar{P})$$

$\left. \begin{array}{l} \therefore A + \bar{A} = 1 \\ \text{Complement Law} \end{array} \right\}$

$$\therefore Z = P\bar{Q}RS + P\bar{Q}R\bar{S} + P\bar{Q}R\bar{S} + P\bar{R}S\bar{Q} + P\bar{R}S\bar{Q} + P\bar{R}\bar{S}\bar{Q} + P\bar{R}\bar{S}\bar{Q} + P\bar{Q}\bar{R}\bar{S} + P\bar{Q}\bar{R}\bar{S}$$

$\underbrace{(P\bar{Q}RS)}$

$$\therefore Z = \sum m(0, 8, 9, 11, 12, 13, 14, 15)$$

(P, Q, R, S)

$\left. \begin{array}{l} \therefore A + A = A \\ \end{array} \right\}$

Thus, the K-Map is given by,

RS		00	01	11	10
PQ		00	01	11	10
		1 0	0 1	0 3	0 2
	01	0 4	0 5	0 7	0 6
11		1 12	1 13	1 15	1 14
10		1 8	1 9	1 11	0 10

K-Map.

$$\therefore Z = \overline{Q} \overline{R} \overline{S} + PQ + PS$$

=> The minimized expression corresponding to the output Z is,

$$Z = P(Q+S) + \overline{Q} \overline{R} \overline{S}$$

Q.4.

$$f(A, B, C, D) = \sum m(2, 3, 8, 10, 11, 12, 14, 15)$$

$$\therefore f = \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}CD + A\bar{B}\bar{C}\bar{D} + A\bar{B}C\bar{D} \\ + A\bar{B}CD + AB\bar{C}\bar{D} + ABC\bar{D} + ABCD$$

\therefore The K-Map is given by.

		AB	00	01	11	10
		CD	00	01	11	10
AB	CD	00	0 ₀	0 ₁	1 ₃	1 ₂
		01	0 ₄	0 ₅	0 ₇	0 ₆
AB	CD	11	1 ₁₂	0 ₁₃	1 ₁₅	1 ₁₄
		10	1 ₈	0 ₉	1 ₁₁	1 ₁₀

K-Map.


$$\therefore f = A\bar{D} + AC + \bar{B}C$$

(Sum of products)

\Rightarrow The minimised expression in the form SOP :

$$f = A(C + \bar{D}) + \bar{B}C$$

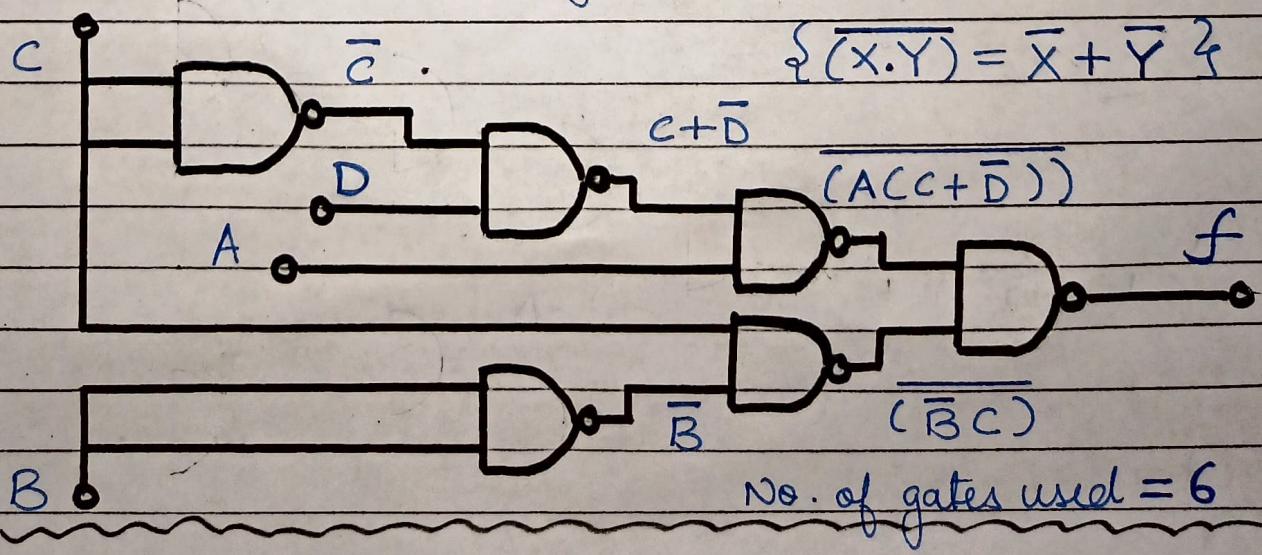\Rightarrow The realization using two input NAND gates,



Q.5.

$$f(w, x, y, z) = wy + xy + \bar{w}xyz + \bar{w}\bar{x}y \\ + xz + \bar{x}\bar{y}\bar{z}$$

$$= wy(x + \bar{x})(z + \bar{z}) + xy(w + \bar{w})(z + \bar{z}) \\ + \bar{w}xyz + \bar{w}\bar{x}y(z + \bar{z}) + \bar{x}\bar{y}\bar{z}(w + \bar{w}) \\ + xz(y + \bar{y})(w + \bar{w}).$$

$$\{ A + \bar{A} = 1 \}$$

$$= wxyz + wxy\bar{z} + w\bar{x}yz + w\bar{x}y\bar{z} \\ + wxyz + wxy\bar{z} + \bar{w}xyz + \bar{w}xy\bar{z} \\ + \bar{w}xyz + \bar{w}\bar{x}yz + \bar{w}\bar{x}y\bar{z} + w\bar{x}\bar{y}\bar{z} \\ + \bar{w}\bar{x}\bar{y}\bar{z} + wxyz + wxy\bar{z} + \bar{w}xyz \\ + \bar{w}xy\bar{z}.$$

Now, $A + A = A$, therefore,

$$= wxyz + wxy\bar{z} + w\bar{x}yz + w\bar{x}y\bar{z} \\ + \bar{w}xyz + \bar{w}xy\bar{z} + \bar{w}\bar{x}yz + \bar{w}\bar{x}y\bar{z} \\ + \bar{w}\bar{x}\bar{y}\bar{z} + w\bar{x}\bar{y}\bar{z} + \bar{w}\bar{x}\bar{y}\bar{z} \\ + w\bar{x}\bar{y}\bar{z} + \bar{w}x\bar{y}\bar{z}.$$

Thus, the K-map is given by,

		yz				
		wx	00	01	11	10
00	1	0	1	1	1	
01	0	4	1	5	1	6
11	0	12	1	13	1	15
10	1	9	1	11	1	14

K-Map

$$f = \sum m(0, 2, 3, 5, 6, 7, 8, 10, 11, 13, 14, 15)$$

\Rightarrow From the K-map,

$$f = \underline{\bar{x}\bar{z} + xz + y}$$

\Rightarrow Therefore, the number of essential prime implicants corresponding to this function is 3 and their complete list is,

$$\underline{y, xz, \bar{x}\bar{z}}$$

$$f = \underline{y + xz + \bar{x}\bar{z}}$$

Q. 6.

\Rightarrow The BCD representation of $(2)_{10}$ is 0010.

\therefore Excess-3 representation is $0010 + 0011 (3)_{10}$.

\therefore Excess-3 representation of $(2)_{10}$ is 0101.

— (1)

\Rightarrow The BCD representation of $(5)_{10}$ is 0101.

\therefore Excess-3 representation is $0101 + 0011 (3)_{10}$.

\therefore Excess-3 representation is 1000. — (2).

Excess-3 addition $(2)_{10} + (5)_{10}$.

$$\begin{array}{r}
 0101 \\
 + 1000 \\
 \hline
 1101 \\
 - 0011 (3)_{10} \quad (\because \text{no carry}) \\
 \hline
 1010 \quad \rightarrow \text{Excess-3}
 \end{array}$$


from (1) and (2).

\Rightarrow The answer for $(2)_{10} + (5)_{10}$ for Excess-3 addition is

1010

Decimal form = $(10)_{10}$

Q. 7.

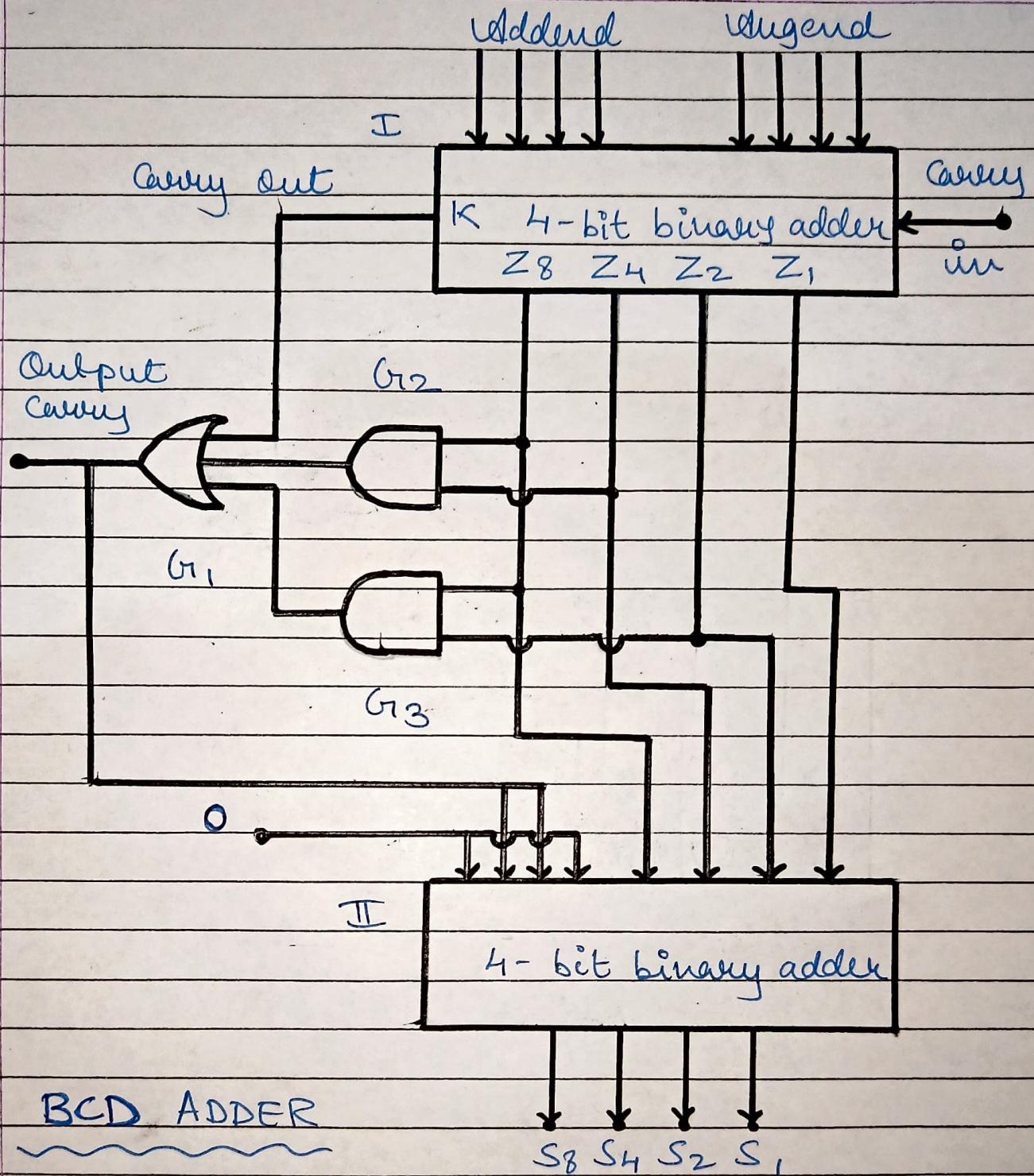

Consider the arithmetic addition of two decimal digits in BCD, together with an input carry from a previous stage. Since each input digit does not exceed 9, the output sum cannot be greater than $9+9+1=19$, the 1 in the sum being input carry.

When we apply two BCD digits to a four-bit binary adder, the adder forms the sum in binary and produce a result that ranges from 0 through 19. These binary numbers are labelled by symbols k, Z_8, Z_4, Z_2, Z_1 . k is the carry, and the subscripts under the letter Z represent the weights 8, 4, 2 and 1 that can be assigned to the four bits in the BCD code.

Now output of AND gate G_2 is $\underline{g_2} = \underline{Z_4} \cdot \underline{Z_8}$ and of AND gate G_3 is $\underline{g_3} = \underline{Z_2} \cdot \underline{Z_8}$.

Output of OR gate G_1 is $\underline{g_1} = \underline{g_2} + \underline{g_3} + k$.
 $\underline{g_1} = \underline{c} = \underline{Z_4} \cdot \underline{Z_8} + \underline{Z_2} \cdot \underline{Z_8} + k$.

Thus, G_1 gives output 1 whenever Z_4 and Z_8 bit are set or, Z_2 and Z_8 bit are set, or the carry k of first adder is 1.

Together this combination gives 1 as output when the sum of the two (BCD)decimal digits and input carry is greater than 9.

When the sum is greater than 9, gate G_1 's output causes $(0\ 110)_2 = (8)_{10}$ to be added to the sum from the first adder using a new second adder. When $\underline{g_1} = \underline{c} = 1$, $(0\ 110)_2$ is added to sum otherwise $(0\ 000)_2$ is added, i.e., sum is unchanged.

The required output is $S_8 S_4 S_2 S_1$. The output

Carry generated by the 4-bit adder II can be ignored, since it supplies information already available at output carry terminal (C). It decimal parallel adder that adds n decimal digits needs n BCD adder stages. The output carry (C) from one stage must be connected to the input carry of the next higher stage adder stage.

$$\underline{C = Z_4 \cdot Z_8 + Z_2 \cdot Z_8 + k}$$

\Rightarrow Thus, this is how the circuit of BCD adder works.

k is 1 for sum from 4-bit adder I,
 $Z_4 \cdot Z_8$ is 1 for sum greater than or equal to 12, $Z_2 \cdot Z_8$ is 1 for sum equal to 11 and 10 (also for 14 and 15). Thus C is 1 for sum from 4-bit adder I greater than 9 (≥ 10).