

Indian Institute of Technology BHU Varanasi, Varanasi
Department of Electronics Engineering
Digital Circuits and Systems (EO-203)

Mid Term Examination, Date: February 28, 2022


Timing: 08:00 Am onwards

Both Part 2 and Part 3


Max mark: 30

Attempt All Questions

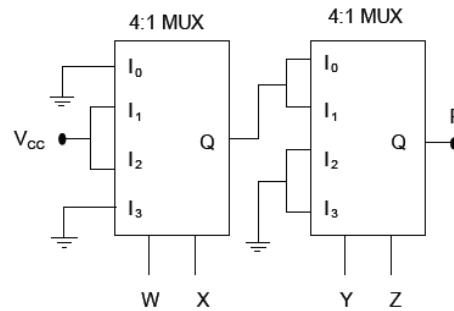- Implement $F(A, B, C, D) = \sum m(0, 1, 5, 6, 8, 10, 12, 15)$ using 8:1 MUX. (4 Marks)
 - Provide the 16 bit 2's complement representation for decimal number (-28). (2 Marks)
 - Convert the binary number 1011 in the form of Gray code. (2 Marks)
- Please derive the minimized Boolean expression corresponding to the output F in below Figure. Please note that W and Y are the MSBs. (4 Marks)



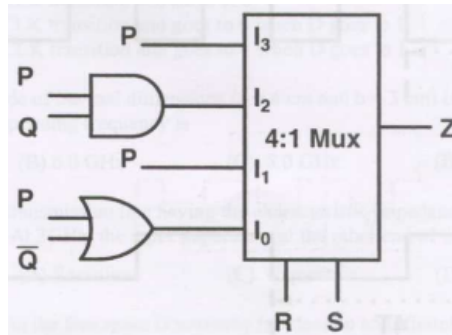- In the below multiplexer circuit, I_0 to I_3 are the inputs, while R and S are the control bits. Please obtain the minimized expression corresponding to the output Z. (4 Marks)



- The Boolean function $f(A, B, C, D) = \sum m(2, 3, 8, 10, 11, 12, 14, 15)$, is given using minterms. Please provide the minimized expression in the form SOP using K-map. Additionally, provide the realization using two input NAND gates. (4 Marks)
- If the Boolean function $f(w, x, y, z) = wy + xy + \bar{w}xyz + \bar{w}\bar{x}y + xz + \bar{x}\bar{y}\bar{z}$. Then, please provide the complete list of essential prime implicants corresponding to this function. (4 Marks)
- Please provide the Excess-3 addition of $(2)_{10} + (5)_{10}$. (2 Marks)
- Please explain the complete circuit diagram of BCD adder. (4 Marks)

Best wishes